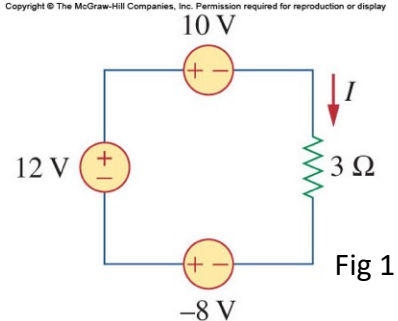




Student ID: _____ Student Name: _____ Group: _____

1) For the circuit in Fig 1, find (a) the voltage across $3\ \Omega$, (b) current I .

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

2) Calculate the equivalent resistance R_{ab} at terminals a-b for Fig 2.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

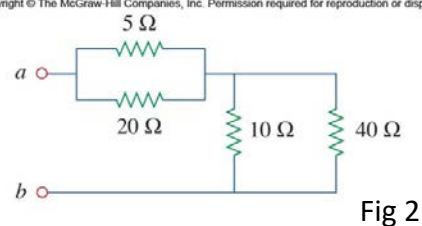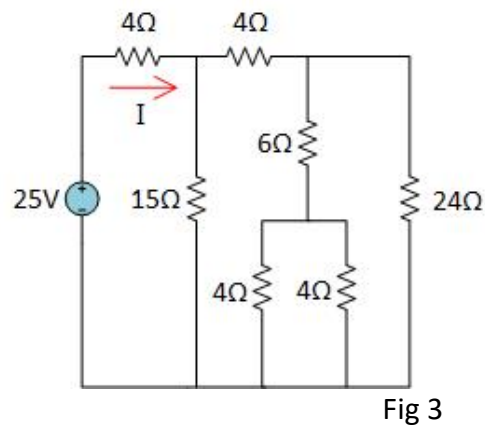3) For the circuit in Fig 3, find the current I . Hint: Find the equivalent resistance seen by the source, and use Ohm's law.

4) For the circuit in Fig 4, given the current directions at node 1 and node 2,

i) Circle the correct nodal equation at node 1.

- (a) $24 = -V_1 - 2V_2$
- (b) $18 = 7V_1 - 2V_2$
- (c) $12 = -V_1 - 2V_2$
- (d) $36 = 7V_1 - 2V_2$

ii) Circle the correct nodal equation at node 2.

- (a) $3V_1 - 5V_2 = 36$
- (b) $3V_1 - V_2 = 36$
- (c) $3V_1 - 5V_2 = -36$
- (d) $3V_1 - V_2 = -36$

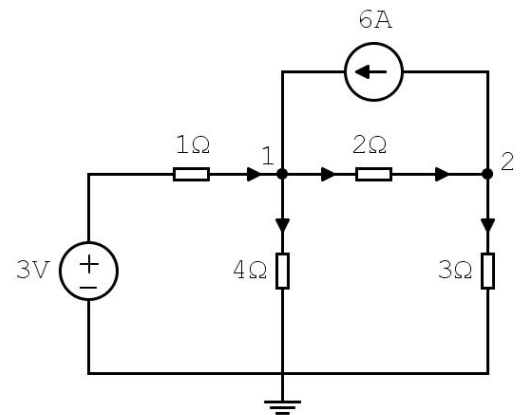


Fig 4

5) By applying nodal analysis at node v_2 of circuit in Fig 5, find v_1 and v_2 .

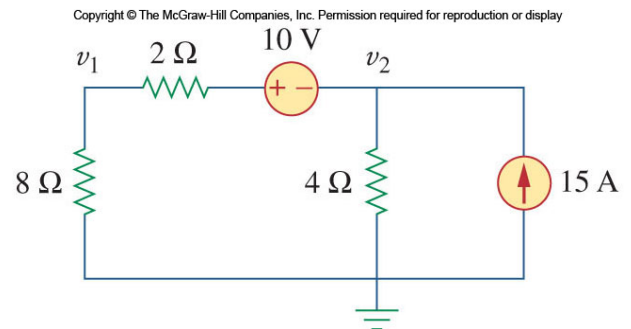


Fig 5

6) For the circuit in Fig 6, obtain the mesh equation at: (No need to solve for variables)

Hint: Assume the voltage across the 4A current source is v

- i) Mesh 1 with final form: $a_1 \cdot i_1 + a_2 \cdot i_2 + a_3 \cdot i_3 = 8 - v$
- ii) Mesh 2 with final form: $c_1 \cdot i_1 + c_2 \cdot i_2 + c_3 \cdot i_3 = -v$
- iii) Mesh 3 with final form: $b_1 \cdot i_1 + b_2 \cdot i_2 + b_3 \cdot i_3 = 0$

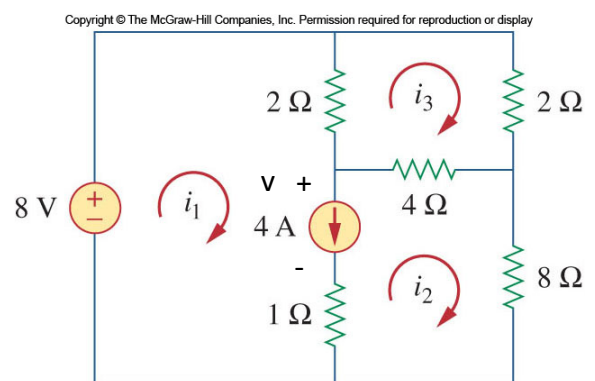


Fig 6